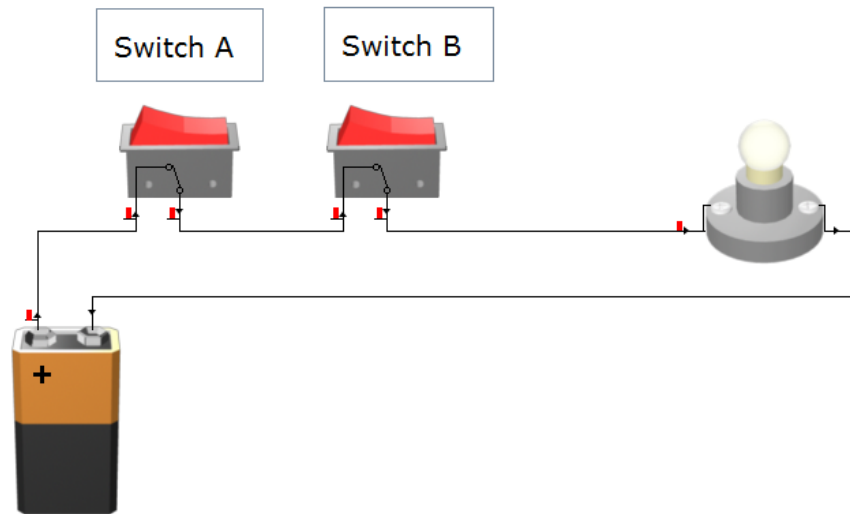


Notice the difference? When both switches are closed, the lamp glows.

This is called a AND circuit. Two switches are connected in series. Both A AND B must be closed for current to flow.



```
If Sw1 = True AND Sw2 = True Then  
    PowerOn = True  
Else  
    PowerOn = False  
End If
```