

Now, the LED is connected backwards.

Notice how I wired the LED. I reversed the power and ground and now it will not light...why not?

