

Here, an LED is powered by the battery through a resistor.

When using a Light-Emitting Diode (LED) you always need a resistor to limit the current. Otherwise it will burn out the LED.

