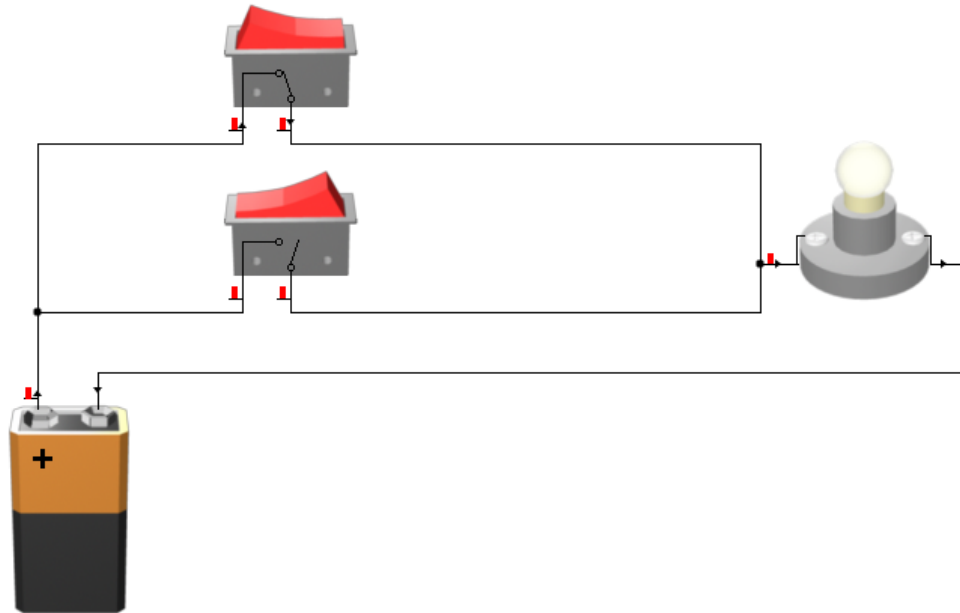


Here two switches are wired in a way that if either one OR both are closed, the lamp lights. This is an OR circuit.

Here we have two switches in parallel. If either switch is closed, the lamp will light. This is called an OR circuit.



```
IF Sw1= True Or Sw2 = True Then  
    PowerOn = True  
Else  
    PowerOn = False  
End If
```