


When a TTL gate changes state, the amount of current that it draws changes rapidly. These changes in current, called switching transients, appear on the power supply line and can cause false triggering of other devices. For this reason, the power bus should be adequately decoupled. For proper decoupling of TTL circuits, connect a 0.01 to 0.1 μF capacitor from VCC to ground near each device to minimize the transient currents caused by device switching and magnetic coupling. These capacitors must be low-inductance, high frequency RF capacitors (ceramic capacitors are preferred). In addition, a large-value (50 to 100 μF) capacitor should be connected from VCC to ground somewhere on the board to accommodate the continually changing ICC requirements of the total VCC bus line. These are generally low-inductance tantalum capacitors.

By-Pass Caps shunt noise to ground. De-coupling caps smoothe signals.

In a common emitter amplifier, a cap can be added to the R_E to trap noise. The cap should have 1/10 the resistance of the parallel resistor.

$$C = \frac{1}{2\pi f X_C} \text{ where } f = \text{line frequency (60Hz)} \text{ and } X_C = \text{reactance at the given frequency}$$

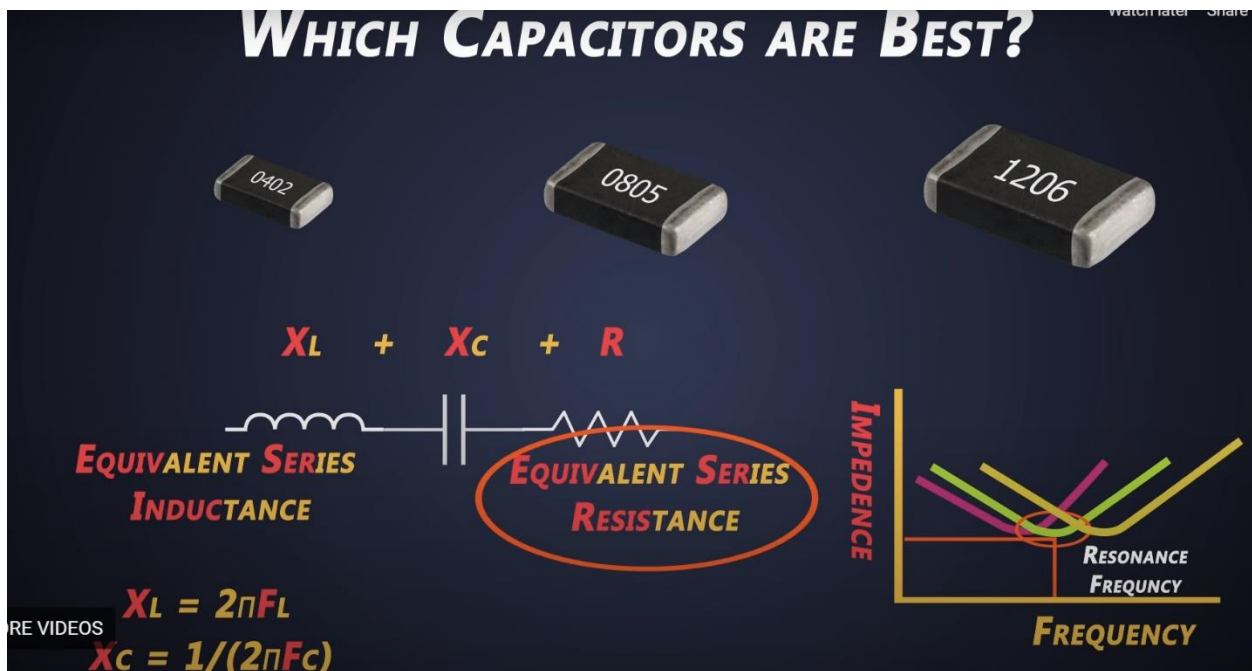At <50MHz signals: 1uF and 10nF and .001uF in parallel work best. Keep the smallest value cap closest to the IC Vcc pin.



A partial list of TTL subfamilies includes:

74xx standard TTL

H 74Hxx High-speed

L 74Lxx Low-power

S 74Sxx Schottky

F 74Fxx Fairchild Advanced Schottky

LS 74LSxx Low-power Schottky

AS 74ASxx Advanced Schottky

ALS 74ALSxx Advanced Low-power Schottky