SALLEN-KEY TOPOLOGY WITH BUTTERWORTH CHARACTERISTIC (R_F/R_I)

66. Low Pass Active Filters - YouTube

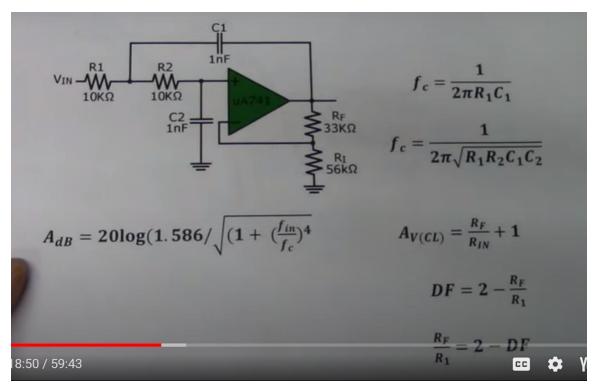


Figure 1: 2-Pole Active Filter. R1 & C2 are one pole and C1 and R2 Comprise the Second pole.

- Butterworth:
 - Flat response
 - o Maximally flat
 - o Phase shift
 - NOT for audio because it produces phase shifting in the output!
- Bessel:
 - \circ $\,$ Good for pulse signals
 - o No phase shift
 - Low roll off
- Chebyshev
 - Rapid roll-off
 - Gain is NOT constant
- Elliptic (Low-pass and notch filter combined)
 - Gain is not constant
 - o Good roll-off

The Damping factor determines the type of filter. It is set by R_F and R_L DF = 2- R_f/R_i (Figure 1).

- Gain of 4dB = Butterworth.
- Gain > 4dB = Chebyshev
- Gain < 4dB = Bessel
- A change in the gain affects the characteristics and damping.

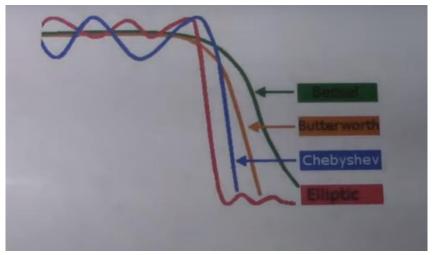


Figure 2: Comparison of Filter Families. Damping Factor Determines the Curve Characteristics

The Butterfield etc. filters REQUIRE a mulit-pole design. Single pole filters do not have a damping factor. A pole represents a resistor and capacitor. In Figure 3, that would be R1 and C1.

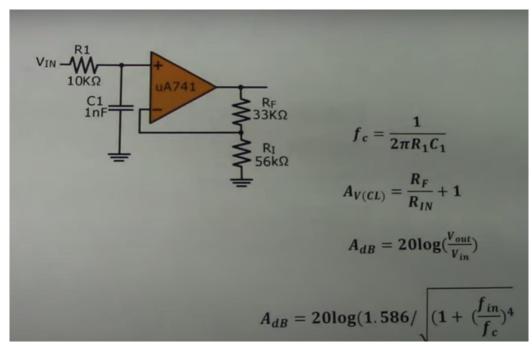


Figure 3: Single Pole Active Low-Pass Filter.

Six-Pole Filter. Each pole provides 20dB roll-off/decade. This filter has 120dB/decade. Resistors in feedback network must be changed in order to maintain 4dB (Butterworth). Gain also increase by 4dB per stage.

Damping factor changes with the number of stages.

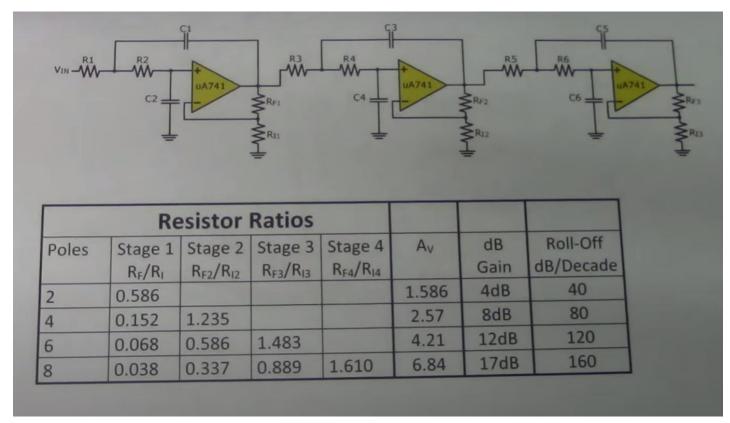


Figure 4: Damping Factor & Resistor Values for Butterworth Family

UNITY GAIN SALLEN-KEY DESIGN

1V in = 1V out.

Use Capacitors to determine damping factor. Ratio of C2/C1 must be .5 for butterworth characteristics. To create a high-pass, just reverse location of resistors and capacitors.

