

UCI STUDY GROUP (2021)

WORKING WITH VOLTAGE DIVIDERS

"A voltage divider is a passive linear circuit that produces an output voltage (V_{out}) that is a fraction of its input voltage (V_1). Voltage dividers are used to make signal level adjustments, for active device and amplifier bias, and for measuring voltages.

[Ohm's Law](#) explains the relationship between voltage, current, and resistance by stating that the current through a conductor between two points is directly proportional to the potential difference across the two points.

A law is relating the voltage difference between two points, the electric current flowing between them, and the resistance of the path of the current. Mathematically, the law states that $V = IR$, where V is the voltage difference, I is the current in amperes, and R is the resistance in ohms. For a given voltage, higher resistance entails lower current flow." ([Digi-Key Electronics](#))

Figure 1 shows a basic divider circuit without any load. Notice both resistors are the same value. In this situation, the output voltage is always $\frac{1}{2}$ of V_1 under NO LOAD. This holds true for any resistor value pairs. The resistor values of R_1 and R_2 , are chosen to limit current in the output. Higher values equates to lower current and visa versa since Ohms law states current $I = \frac{E}{R}$.

But what happens when we *do* have a load connected? Well, Figure 2 shows a circuit but with a load (R_3) connected. This is because R_2 and R_L are connected in parallel.

Whereas resistors in series form a total resistance that equals their sum, resistors in parallel combine to reduce the total resistance. This is called **equivalent resistance**.

The total resistance is always less than the smallest resistor. In our case we only have two resistors so, equivalent resistance is calculated with this formula:

$$R_{EQ} = \frac{100 \times 1000}{1100} = 90.9 \text{ ohms.}$$

Therefore, $R_2 || R_3$ in parallel is equivalent to an R_2 of 90.9 Ω instead of the 100 Ω . This explains why the V_{OUT} is less than the 10 volts we would expect with two equal value resistors. When resistors in parallel are shown in formulas, they are denoted like this: $R_2 || R_L$ where the "||" symbol means "in parallel with".

When more than 2 resistors are in parallel, we use this formula:
$$R_T = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}}$$

When only 2 resistors are in parallel, use this formula:
$$R_{EQ} = \frac{R_1 \times R_2}{R_1 + R_2}$$

Fortunately, there are online [calculators](#) that compute this for us.

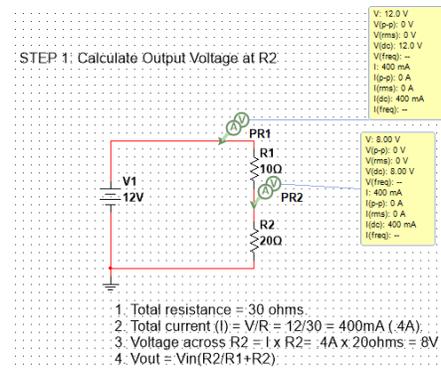


Figure 1: Simulation of simple voltage divider with NO load. Voltage is half the V_{in} .

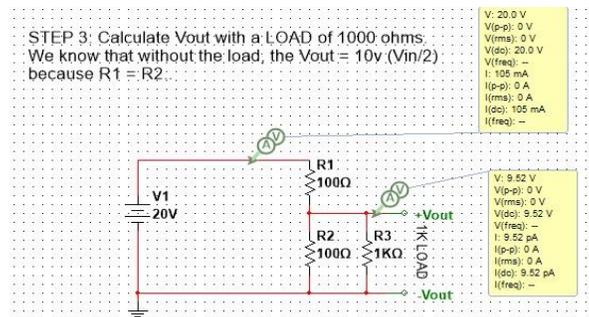


Figure 2: Simulation WITH a load. Notice the change in voltage. R_2 and R_L are in parallel which lowers the equivalent resistance.

Look at the circuit in Figure 3. I want you to see the steps taken to analyze this circuit. I also show how this circuit wastes a lot of energy. We will see how to fix that very soon.


TIP: Recall that we can use a simpler formula when only 2 resistors are in parallel:

$$R_{EQ} = \frac{R1 \times R2}{R1 + R2}$$

$$\text{So, } R_{EQ} = \frac{100 \times 1000}{1100} = 90.9 \text{ ohms}$$

$$\text{So } V_{out} = V_{in} \left[\frac{90.9}{90.9 + 100} \right] = 9.95 \text{v}$$

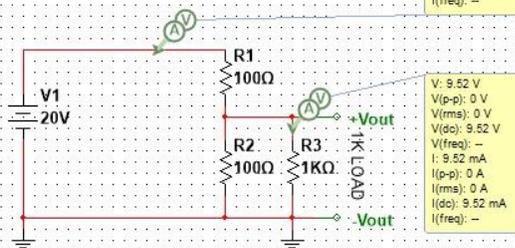STEP 4: Calculate V_{out} with a LOAD of 1000 ohms. We know that without the load, the $V_{out} = 10\text{v}$ ($V_{in}/2$) because $R1 = R2$.




1. Now, $R2$ & $R3$ are in parallel so the equivalent resistance will be lower than the smallest value resistor. So it will be less than 100 ohms.
2. Calculate the equivalent resistance or $R2 || R3$. The "||" means "in parallel with". Resistors in parallel formula = $1/[1/R2 + 1/R3] = 1/[1/100 + 1/1000] = 1/.01 + .001 = 90.9$ ohms.
3. $V_{out} = V_{in} * [R_{equiv}/R1 + R_{equiv}]$. That means $V_{out} = 20 \times [90.9/90.9 + 100] = 9.52\text{V}$.
4. When the $R3$ load is at least $100 \times > R2$, the V_{out} does not change so much. If $R3$ was 10 ohms, Equivalent resistance is now $1/[1/100 + 1/10] = 9.09$ ohms
5. Now, $V_{out} = 20 \times [9.09/9.09 + 100] = 1.67$ volts. If the load is 10K, $V_{out} = 9.95!$
6. Total current in the circuit = V/R or $20/[90.9 + 100] = \sim 104\text{mA}$. The current through $R3 = 9.52/1000 = 9.5\text{mA}$. The load is pulling only 9% of the $V1$ so a lot of current is wasted and goes up in heat and runs down the battery.

Figure 3: Equivalent resistance for $R2$ and $R3$ wastes energy.

Figure 4 shows how to make the circuit more efficient by simply replacing $R2$ with the 1K load device ($R3$) as shown. This not only simplifies the circuit, but it also uses significantly less current.

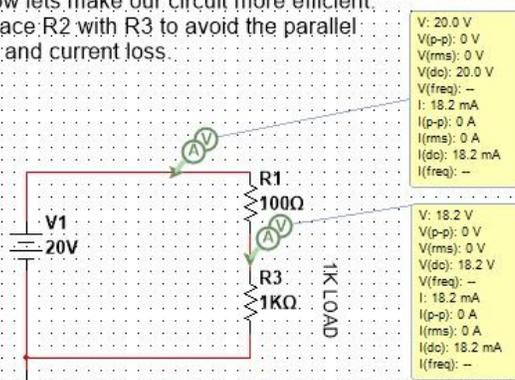STEP 5: Now lets make our circuit more efficient. We will replace $R2$ with $R3$ to avoid the parallel resistances and current loss.



1. Now, our calculations are simplified. $V_{out} = V_{in} [1K / 1K + 100] = 20(.909) = 18.2$ volts.
2. Calculate the total current: $I = V/R$ so $I = 20/1100 = 18.2\text{mA}$.
3. Calculate current consumed by $R3$: $I = 18.2/1000 = 18.2\text{mA}$. So all of the current supplied by the battery flows through the load and we have a very efficient circuit.

Figure 4: Efficient version with the load replacing $R2$.

Voltage Dividers with Three Matching Resistors

There are many situations where we need two different voltages from our divider. The 555 timer is such an example. When we discuss the 555 timer IC, you will discover how clever this divider is used to monitor the charge across a capacitor.

Try to picture a situation where you have a 9v power source and you need 6v to power a servo and 3v to power a sensor board. Rather than adding a large power supply to your project, you can use a voltage divider configured like the one in Figure 5. A word of caution. Never use a divider to supply high amounts of current. These are perfectly suited to working with Arduino projects and other low voltage, low current circuits. Resistors are not efficient, they convert energy into heat, and cannot regulate voltage if the V_{in} goes up or down. These never take the place of a linear regulator! This configuration divides the V_{in} into thirds. The 9v supply provides 6v and 3v for you project needs. Let's figure out how this works in more detail.

In previous discussions, we learned that in series circuit, the current that flows through each component is the same. There is only one path for it to flow. However, the voltage *across* each resistor is related to the resistor's value. When all the resistors are the same value, then the voltage across them is equal and the V_{in} is divided equally across them. Also, the total resistance = $R_1 + R_2 + R_3$ which equals 3K in this case. The total current in the circuit is therefore $I = 9/3000 = .003A$ or 3mA as shown in Figure 5.

Since $V = IR$, the voltage across each resistor = $.003A \times 1000\Omega = 3v$. The voltage law says *all* voltages applied to a circuit are consumed by the components. Take your voltmeter and place the probes across each individual resistor and you will read 3v. Since R_1 drops 3v we read 9-3 or 6v at the bottom of R_1 . We read 3v at the top of R_3 because $R_1+R_2 = 6K\Omega$ and thus twice as much voltage is consumed.

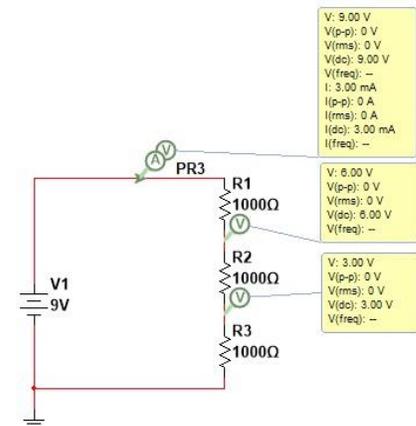


Figure 5: Three identical resistors can be used as a 1/3 and 2/3 voltage divider when two different voltages are required.