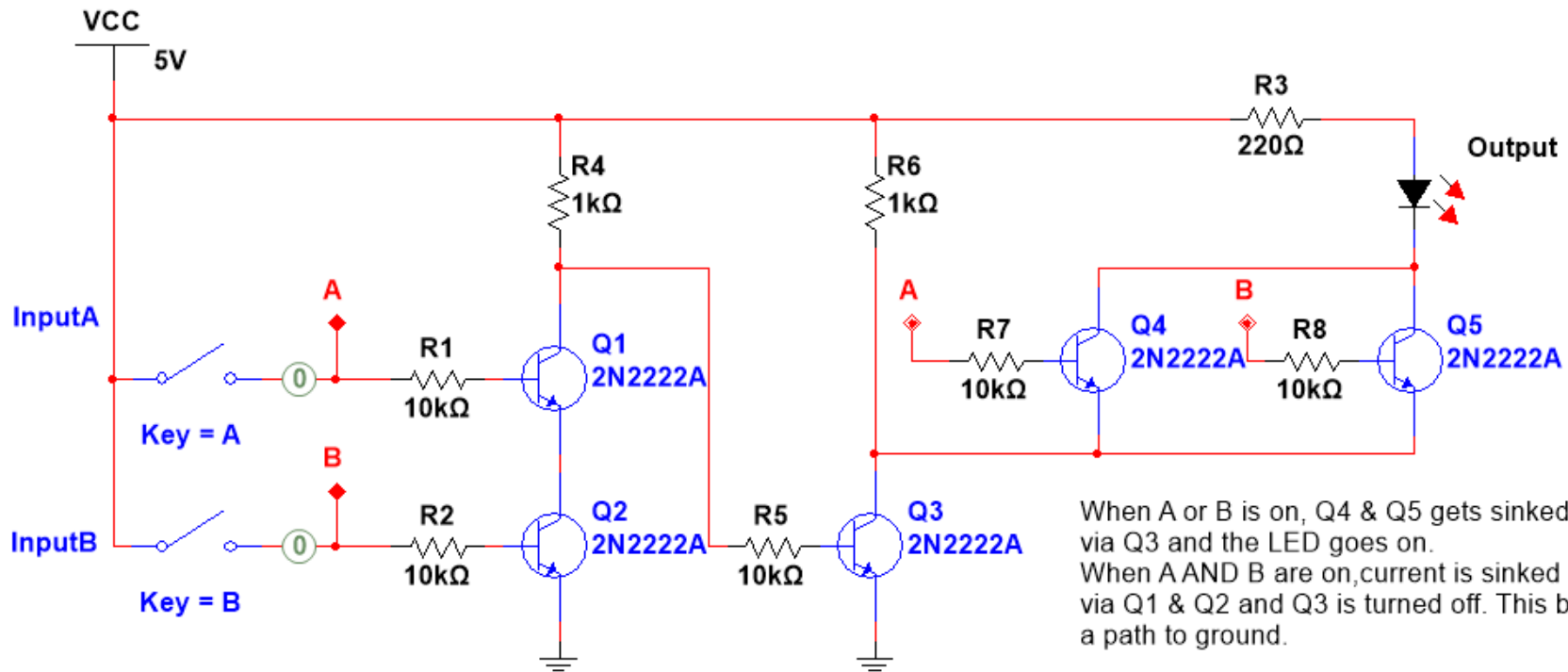


XOR Logic Gate Using 2N2222 Transistors




When A or B is on, Q4 & Q5 gets sinked via Q3 and the LED goes on.
 When A AND B are on, current is sinked via Q1 & Q2 and Q3 is turned off. This blocks a path to ground.

Q1 & Q2 function as a NAND gate
 Q4 & Q5 function as a OR gate.
 Q3 provides a way to sink Q4 & Q5

$$R3 = 5V - 1.7v / .015A = 220ohms$$

Inputs		Outputs
X	Y	Z
0	0	0
0	1	1
1	0	1
1	1	0

Electronics Workbench 801-111 Peter Street Toronto, ON M5V 2H1 (416) 977-5550		 A NATIONAL INSTRUMENTS COMPANY
Title: Digital Logic	Desc.: XOR Gate Using 2N2222 Transistors (NAND + OR)	
Designed by: Ron Kessler	Document No: 1	Revision: 1
Checked by:	Date: 8/7/2022	Size: A
Approved by:	Sheet 1 of 1	

